

Exercise MCQs

Sr. No.	Questions	A	B	C	D
1	An electric current in conductors is due to the flow of	positive ions	negative ions	positive charges	✓ free electrons
2	What is the voltage across a $6\ \Omega$ resistor when 3 A of current passes through it?	2 V	9 V	✓ 18 V	36 V
3	What happens to the intensity or the brightness of the lamps connected in series as more and more lamps are added?	Increases	✓ decreases	remains the same	cannot be predicted
4	Why should household appliances be connected in parallel with the voltage source?	to increase the resistance of the circuit	to decrease the resistance of the circuit	✓ to provide each appliance the same voltage as the power source	to provide each appliance the same current as the power source
5	Electric potential and e. m. f	are the same terms	✓ are the different terms	have different units	both (B) and (C)
6	When we double the voltage in a simple electric circuit, we double the	✓ current	power	resistance	both (a) and (b)
7	If we double both the current and the voltage in a circuit while keeping its resistance constant, the power	remains unchanged	halves	doubles	✓ Quadruples OR become four times
8	What is the power rating of a lamp connected to a 12 V source when it carries 2.5 A?	4.8 W	14.5 W	✓ 30 W	60 W
9	The combined resistance of two identical resistors, connected in series is $8\ \Omega$. Their combined resistance in a parallel arrangement will be	$2\ \Omega$	✓ $4\ \Omega$	$8\ \Omega$	$12\ \Omega$

Additional MCQs

Sr. No.	Questions	A	B	C	D
1	Formula of current is	$I = Qt$	$\checkmark I = \frac{Q}{t}$	$I = \frac{t}{Q}$	All of these
2	SI unit of current is	Coulomb	$\checkmark$ Ampere	Volt	Farad
3	The unit of potential difference is	Joule	Coulomb	Farad	$\checkmark$ Volt
4	Formula of e. m. f	$E = \frac{J}{Q}$	$E = \frac{W}{I}$	$\checkmark E = \frac{W}{Q}$	$E = \frac{W}{Q}$
5	The unit of e.m.f in SI system is equal to	J	Jm^{-1}	JS^{-1}	$\checkmark JC^{-1}$ OR V(volt)
6	An ideal volt meter has resistance	Very low	$\checkmark$ Very large	Low	Zero
7	Specific resistance of copper is	$1.7 \times 10^{-8} \Omega m$	$\checkmark 1.69 \times 10^{-8} \Omega m$	$100 \times 10^{-8} \Omega m$	$3500 \times 10^{-8} \Omega m$
8	Specific resistance of silver is	$\checkmark 1.7 \times 10^{-8} \Omega m$	$1.69 \times 10^{-8} \Omega m$	$100 \times 10^{-8} \Omega m$	$3500 \times 10^{-8} \Omega m$
9	Specific resistance of aluminium is	$\checkmark 2.75 \times 10^{-8} \Omega m$	$5.25 \times 10^{-8} \Omega m$	$9.8 \times 10^{-8} \Omega m$	$10.6 \times 10^{-8} \Omega m$
10	Unit of resistance is	F(Farad)	C(Coulomb)	$\checkmark \Omega$ (Ohm)	V(Volt)
11	When resistances are connected in series, the current passing through them is	Different	Zero	$\checkmark$ Same	None
13	Which one is OHMIC in nature?	Thermister	Filament lamp	$\checkmark$ Fixed resistor	Variable resistor
14	Mathematical form of joule's law	$W = I^2 R t$	$\checkmark W = I R^2 t$	$W = I^2 R^2 t$	$W = I R t$
15	Which one is not true for power?	$P = I^2 R$	$P = \frac{QV}{t}$	$\checkmark P = I R$	$P = I V$
16	The unit of electric power is	Ampere	Joule	$\checkmark$ Watt	Volt
17	1kWh is equal to	3 MJ	$\checkmark 3.6$ MJ	2 MJ	2.6 MJ
18	SI unit of electric power is	$1 W = Js$	$\checkmark 1 W = Js^{-1}$	$1 W = J^{-1}s^{-1}$	$1 W = J^{-1}s$
19	Potential of neutral wire	$\checkmark 0 V$	1 V	100 V	220 V
20	An ideal ammeter has resistance	Very low	Very large	Low	$\checkmark$ Zero
21	Two resistances 6 k Ω and 12k Ω are connected in parallel across a 6 V battery. The potential difference across 6 k Ω resistance is ____ volts.	2	4	6 $\checkmark$	12
22	A 100 Watt bulb is connected to 250 V supply the current flowing through the bulb is	0.4 A $\checkmark$	2.5 A	4.8	14.5 A
23	The equivalent resistance of two resistor of 6 k Ω and 4k Ω are connected in series across 10 V abttery	$\checkmark 10 k\Omega$	2 k Ω	$\frac{12}{5} k\Omega$	$\frac{5}{12} k\Omega$